

## Quiz 10A


PHYSICS 208, WINTER 2016

SECTION:

NAME:

**Instructions:** *Carefully* read each question and write your work in a neat and organized manner.

Figure 1: A Simple RLC Circuit

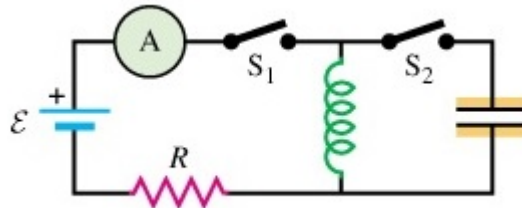

### The RLC Circuit

The circuit in Figure 1 has an inductor of self-inductance  $L$  and a capacitor of capacitance  $C$ . **(A)** [80 pts] Using Kirchoff's loop rule, write an equation that describes how the charge on the capacitor  $q$  changes with time, if  $S_1$  is open and  $S_2$  is closed. Assume that a moment earlier, a steady current  $I_0$  was established with  $S_1$  closed and  $S_2$  open. **(B)** [20pts] Sketch a graph of current versus time to represent the  $S_1$  open and  $S_2$  closed case.